Template Week 2 – Logic

Student number:570350

Assignment 2.1: Parking lot

Which gates do you need?

We need 2 AND gates.

Complete this table

Parking lot 1	Parking lot 2	Parking lot 3	Result (full)
0	0	0	0
0	0	1	0
0	1	0	0
1	0	0	0
1	1	0	0
0	1	1	0
1	0	1	0
1	1	1	1

Assignment 2.2: Android/iPhone

Which gates do you need?

We need to use XOR gate

Complete this table

Android phone	iPhone	Result (Phone in possession)
0	0	0
1	0	1
0	1	1
1	1	0

Assignment 2.3: Four NAND gates

Complete this table


Α	В	Q
0	0	0
1	0	1
0	1	1
1	1	0


How can the design be simplified?

Assignment 2.4: Getting to know Logisim evolution

Screenshot of the design with your name and student number in it:

Ege Tugal 570350

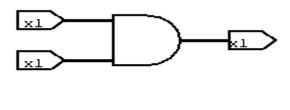


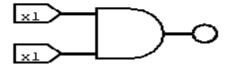

Assignment 2.5: SR Latch


Screenshot SR Latch in Logisim with your name and student number:

Ege Tugal 570350

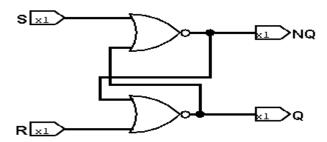

Assignment 2.6: Vending Machine

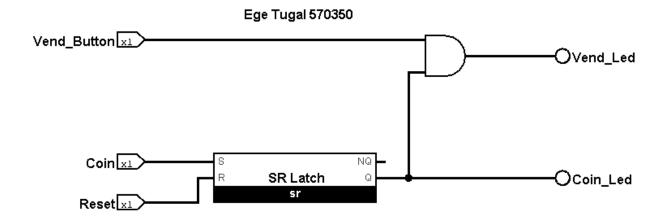Screenshot Vending Machine in Logisim with your name and student number:



Bonus point assignment - week 2


Create a java program that accepts user input and presents a menu with options.


- 1. Is number odd?
- 2. Is number a power of 2?
- 3. Two's complement of number?

Implement the methods by using the bitwise operators you have just learned.

Organize your source code in a readable manner with the use of control flow and methods.

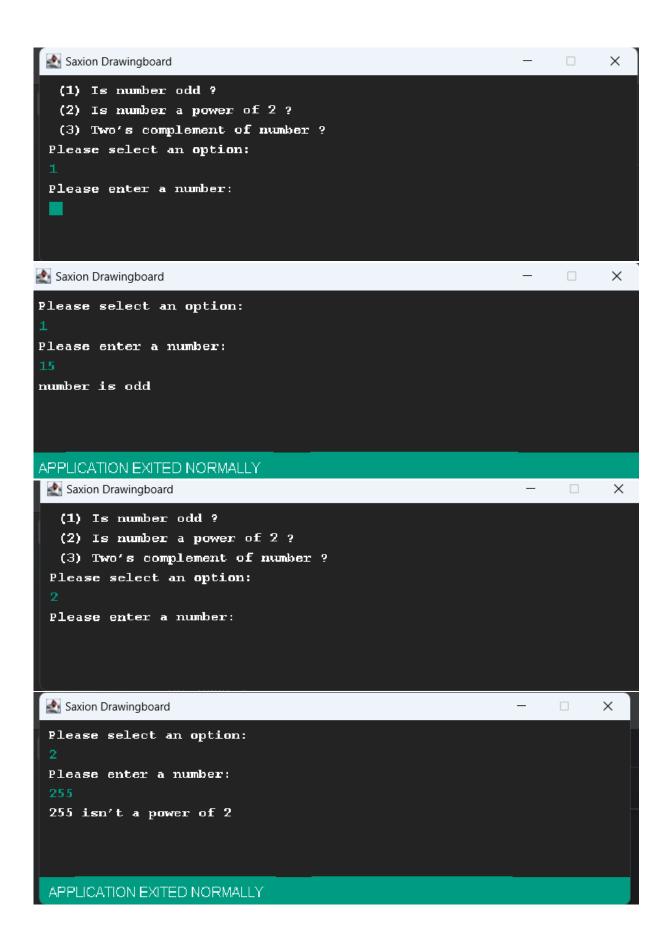Paste source code here, with a screenshot of a working application.



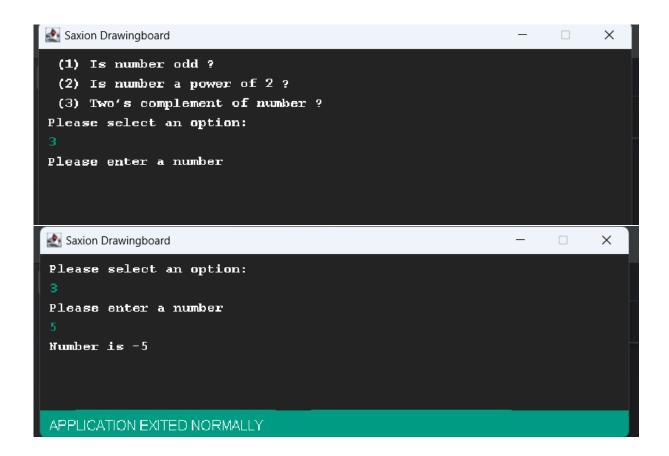

Ready? Then save this file and export it as a pdf file with the name: week2.pdf